

# NTI Project Documentation

---

## **Custom APB UART IP**

**Prepared by:**

**Dina Amgad**

**August /September 2025**

## 1. Introduction

The **APB UART** combines the standard functionality of a Universal Asynchronous Receiver/Transmitter with the accessibility of an AMBA APB slave interface. In normal operation, the UART transmitter (Tx) begins in the **IDLE state**. When the processor writes data into the `TX_DATA` register via the APB bus and sets the `tx_en` bit in `CTRL_REG`, the Tx appends a **start bit** (logic 0), shifts out the data bits one by one (5–8 bits depending on the frame), and finally sends one or more **stop bits** (logic 1). Meanwhile, the receiver (Rx) also starts in **IDLE** until a falling edge is detected on the input line. Once a start bit is recognized and the `rx_en` bit is enabled, the Rx samples the incoming bits at precise baud intervals, reconstructs the frame, and stores the received data into the `RX_DATA` register. Status information such as `tx_busy`, `tx_done`, `rx_busy`, `rx_done`, or `rx_error` is updated automatically in the `STATS_REG`. Through the APB wrapper, the processor can perform simple **read/write transactions** (`PSEL`, `PENABLE`, `PWRITE`, `PWDATA`, `PRDATA`) to configure, monitor, and exchange data, making the UART both **easy to control** and **fully integrable** into a system-on-chip.

## 2. Design Analysis

The proposed design integrates a **Universal Asynchronous Receiver/Transmitter (UART)** with an **AMBA APB slave wrapper**, enabling the UART to be controlled and accessed by a processor in a system-on-chip environment. The implementation is divided into modular components for clarity and reusability:

### *Top-Level APB UART Wrapper*

The `apb_uart` module serves as the integration point between the APB bus and the UART datapath. It provides **register-mapped access** to control signals, data registers, and status flags. The APB interface supports standard read/write operations through `PSEL`, `PENABLE`, `PWRITE`, `PWDATA`, and `PRDATA`. A `PREADY` signal is asserted to acknowledge completed transactions.

- **Control Register (0x00):** Contains enable and reset bits (`tx_en`, `rx_en`, `tx_rst`, `rx_rst`).
- **Status Register (0x01):** Exposes UART activity and error flags (`rx_busy`, `tx_busy`, `rx_done`, `tx_done`, `rx_error`).
- **TX Data Register (0x02):** Holds outgoing data written by the processor and triggers a transmission.
- **RX Data Register (0x03):** Stores the last successfully received byte.
- **Baud Divider Register (0x04):** Configures baud rate for the UART.

This memory-mapped structure makes the UART highly configurable and easy to integrate into a processor-controlled environment.

### *Baudrate Generator*

The `baudrate_gen` module ensures accurate bit timing for UART communication. It divides the system clock (`CLK_FREQ = 100 MHz`) to produce sampling ticks at **16× the baud rate**, supporting reliable oversampling in the receiver. The tick output synchronizes both the transmitter and receiver FSMs.

### *UART Transmitter (TX)*

The `uart_tx` module implements a finite state machine with four states:

- **IDLE:** Line held high until transmission begins.
- **START:** A start bit (0) is transmitted for one baud interval.
- **DATA:** Data bits are shifted out least significant bit first at each baud interval.
- **STOP:** One or more stop bits (1) are sent before returning to IDLE.

The transmitter asserts `tx_busy` while active and `tx_done` once transmission completes. Data is loaded from the APB interface, and a one-cycle `tx_start_pulse` initiates the process.

### *UART Receiver (RX)*

The `uart_rx` module mirrors the Tx structure but works in the opposite direction. It uses **oversampling (16×)** to detect the falling edge of the start bit, sample data in the middle of each bit period, and validate the stop bit. Its FSM has four states:

- **IDLE:** Waiting for start bit detection.
- **START:** Verifies the start bit midpoint.
- **DATA:** Shifts in each received bit sequentially.
- **STOP:** Confirms a valid stop bit; if incorrect, `rx_error` is asserted.

Upon successful reception, the parallel data is output through `dout` and captured by the APB wrapper in `RX_DATA`. Status signals (`rx_busy`, `rx_done`, `rx_error`) provide system-level feedback.

### *System-Level Integration*


The APB UART wrapper coordinates these submodules into a **coherent communication unit**:

- The **baudrate generator** provides the timing backbone.
- The **Tx and Rx modules** perform serial/parallel conversion.
- The **APB logic** handles register-level interfacing, ensuring software can control and monitor UART without dealing with low-level timing details.


This modular architecture makes the design scalable, reusable, and easy to extend (e.g., adding FIFOs or parity support)

### 3. State Diagrams

#### 1. RX

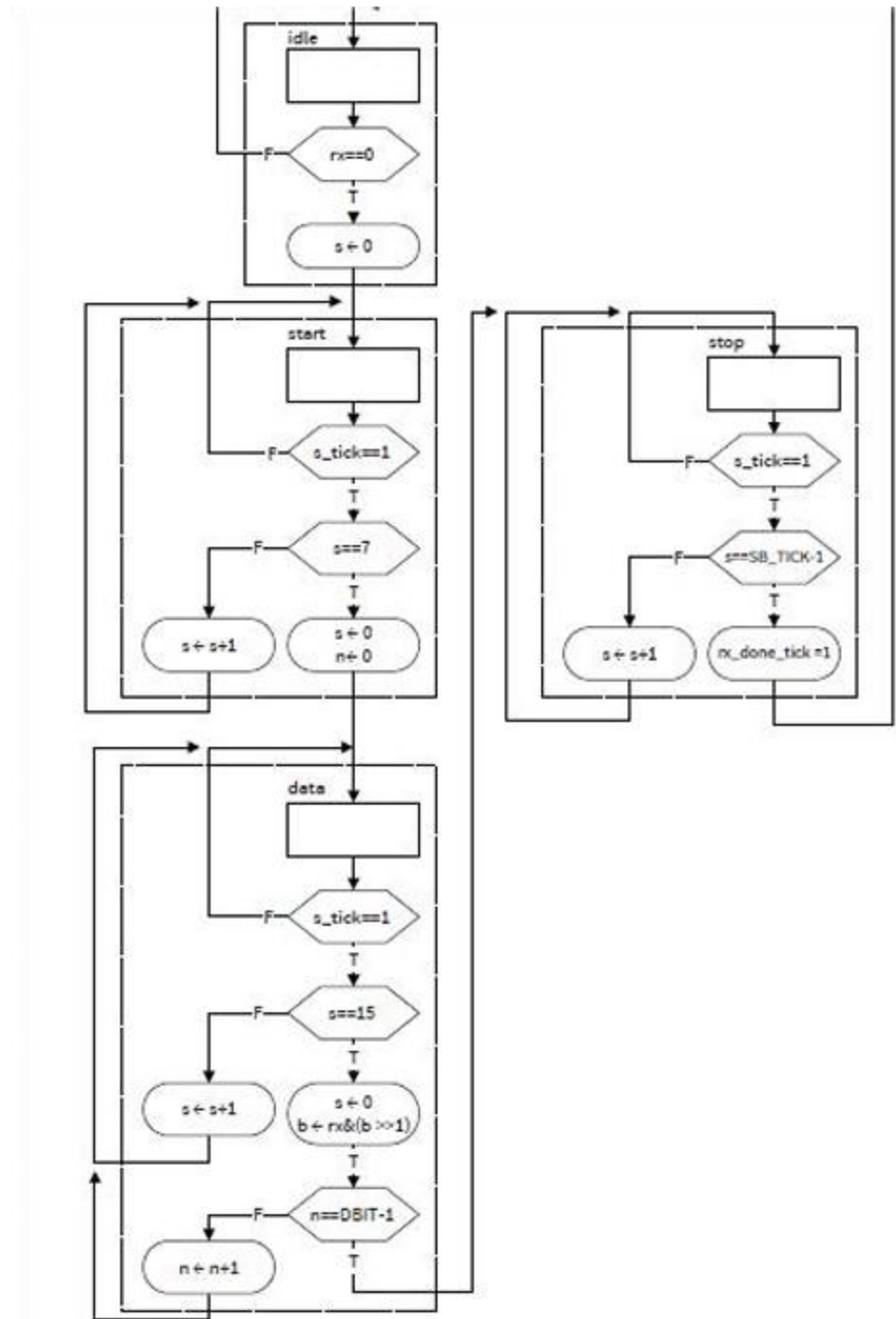

## 2. TX

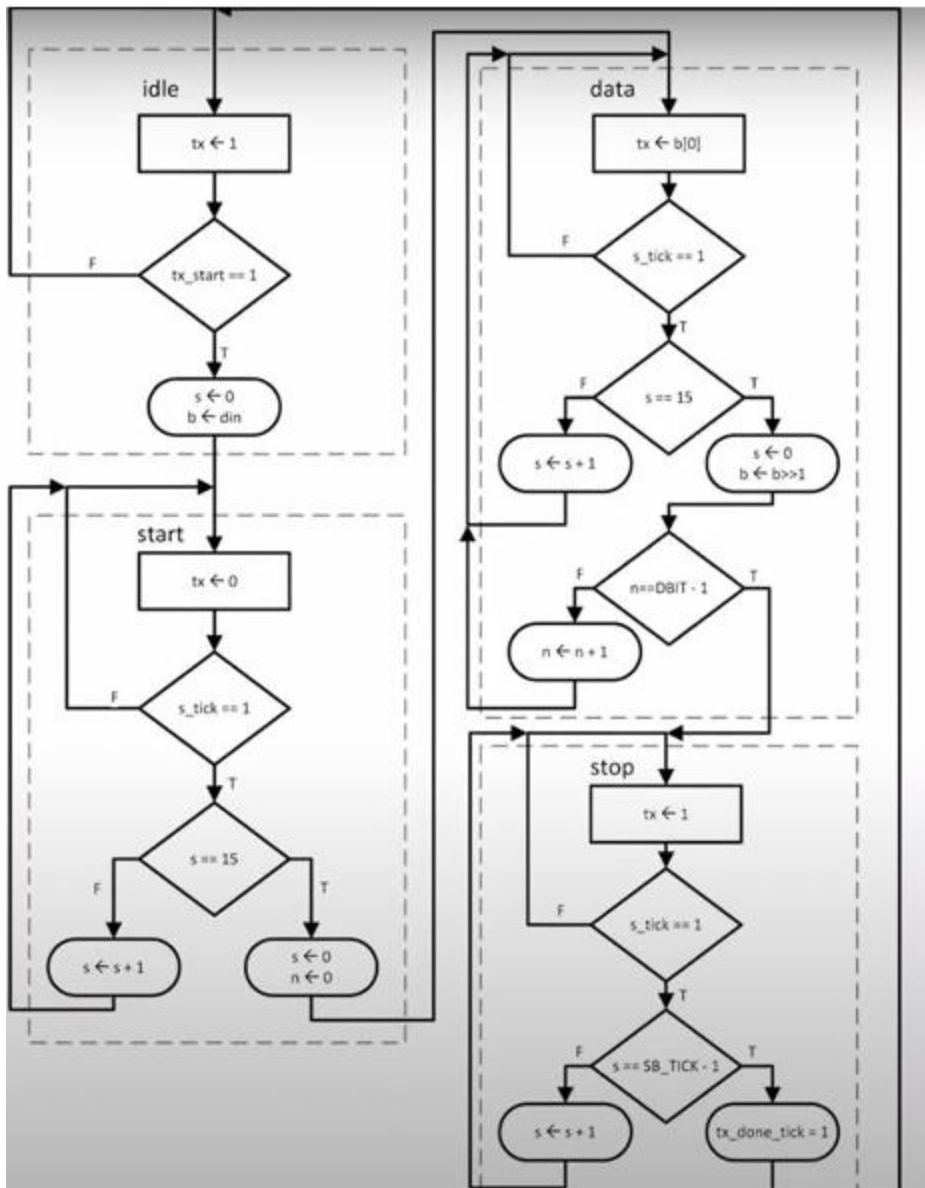

## 4. Design Decisions

During the design and implementation of the APB UART wrapper, several architectural and functional choices were made to balance **simplicity, reliability, and SoC integration**:

### 3. Modular Structure

- The design was divided into independent modules: `uart_tx`, `uart_rx`, `baudrate_gen`, and the `apb_uart` wrapper.
- This approach improves readability, simplifies debugging, and allows individual modules to be reused or replaced.

### 4. FSM-Based Transmitter and Receiver

- Both Tx and Rx were implemented using **finite state machines (FSMs)** with well-defined states: IDLE, START, DATA, STOP.
- FSMs ensure predictable operation, easy timing control, and straightforward error handling.

### 5. 16x Oversampling in Receiver

- The receiver samples incoming data 16 times per bit period.
- This choice increases tolerance to clock mismatches and noise, ensuring robust detection of start, data, and stop bits.

### 6. Memory-Mapped Register Interface via APB

- Control, status, and data registers were mapped into the APB address space (`CTRL_REG`, `STATS_REG`, `TX_DATA`, `RX_DATA`, `BAUDDIV`).
- This makes the UART easily programmable by the CPU through simple read/write transactions without requiring direct timing management.

### 7. Reset and Enable Controls

- Separate reset (`tx_rst`, `rx_rst`) and enable (`tx_en`, `rx_en`) signals were provided.
- This allows software to reset and reinitialize transmitter or receiver modules independently, ensuring clean recovery from errors or abnormal states.

### 8. Baudrate Generator with Divider Register

- A dedicated baudrate generator was chosen instead of relying on fixed timing.
- An optional `bauddiv_reg` provides flexibility to support multiple baud rates, enhancing portability across different applications.

### 9. Status Monitoring for Debug and Synchronization

- Status flags (`tx_busy`, `tx_done`, `rx_busy`, `rx_done`, `rx_error`) were included to help the processor track the progress of transmission/reception.
- These signals also assist in debugging and enable efficient polling-based communication without interrupts.

### 10. Scalability and Future Extensions

- The current design prioritizes **simplicity** (no FIFOs, no parity bit), but the modular approach allows easy extension to support features such as:
  - Transmit/receive FIFOs for buffering.
  - Parity generation/checking for error detection.

- Interrupt-based operation for efficient CPU interaction.



## 5. Verification Strategy

To ensure the correctness of the APB UART design, a **modular testbench-based verification strategy** was adopted. The provided `uart_tb` integrates the **baudrate generator**, **UART transmitter**, and **UART receiver** in a loopback configuration, where the Tx output is directly connected to the Rx input. This setup verifies end-to-end communication without requiring external hardware.

The strategy consists of the following key steps:

### 1. Clock and Reset Generation

- A 100 MHz clock is generated (`always #5 clk = ~clk`).
- Reset signals (`reset`, `tx_rst`, `rx_rst`) are asserted at the start to initialize all modules into a known state.

### 2. Module Instantiation

- `baudrate_gen` produces timing ticks for synchronization.
- `uart_tx` and `uart_rx` are instantiated with consistent data width and oversampling factor (`SB_TICK = 16`).
- The Tx output (`tx`) is looped back to the Rx input, enabling direct self-checking.

### 3. Transmit and Receive Flow

- After initialization, both Tx and Rx are enabled (`tx_en = 1`, `rx_en = 1`).
- A test byte (`0xC1`) is loaded into the transmitter, and a `tx_start` pulse triggers transmission.
- The receiver captures the incoming data, reconstructs the frame, and asserts `rx_done`.

### 4. Result Monitoring and Self-Check

- The testbench prints the transmitted and received values using `$display`.
- A **PASS/FAIL condition** is automatically checked:
  - PASS if `rx_data == tx_data` and `rx_error == 0`.
  - FAIL otherwise, reporting a mismatch or framing error.

### 5. Error Detection

- The `rx_error` flag is monitored to validate stop-bit detection and detect potential framing errors.

### 6. Automation and Termination


- The testbench runs until communication completes, then issues a `$finish` command after a short delay.
- This ensures repeatable simulations with clear outcome reporting.

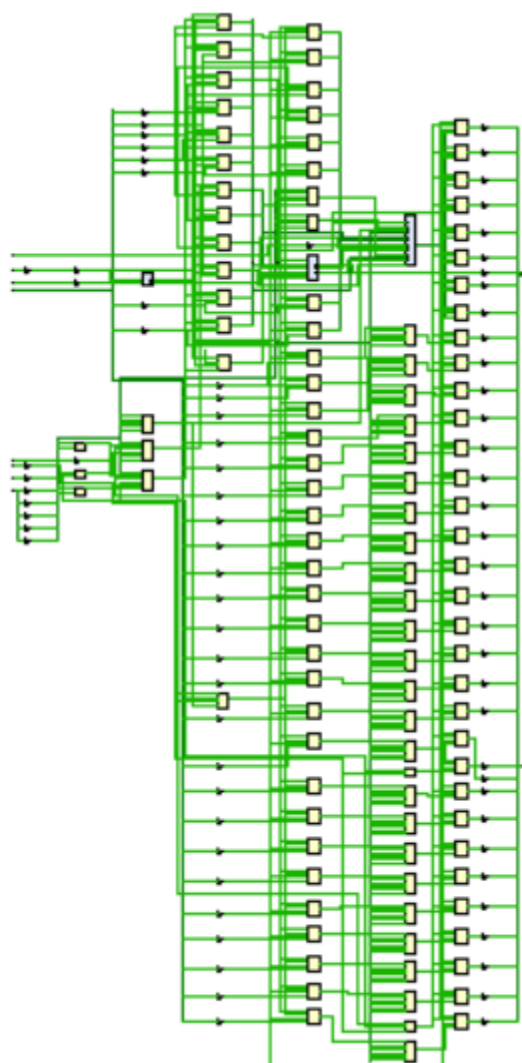
### Future Extensions


The current verification verifies **basic UART loopback**. Additional strategies can include:

- Back-to-back transmissions to test continuous operation.





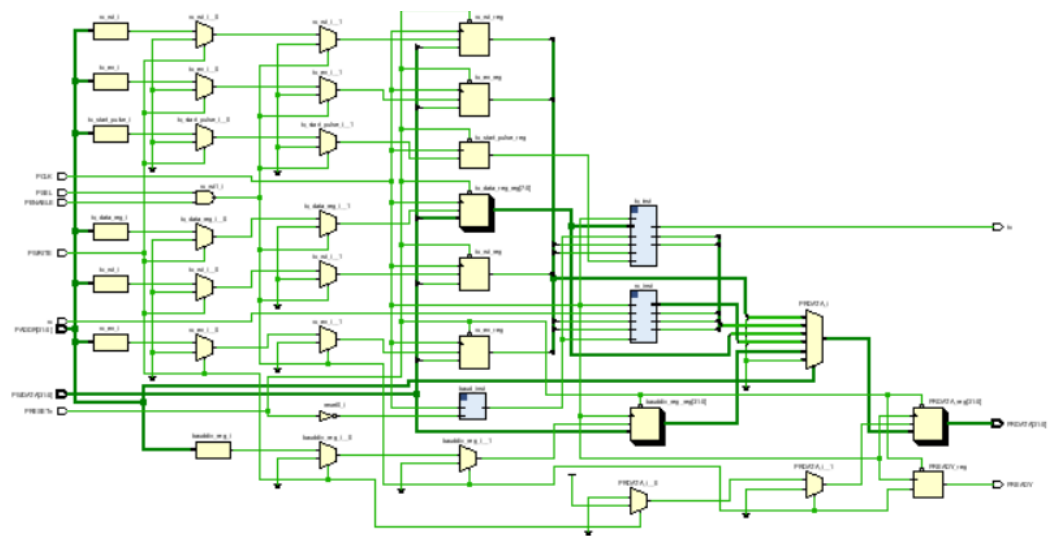

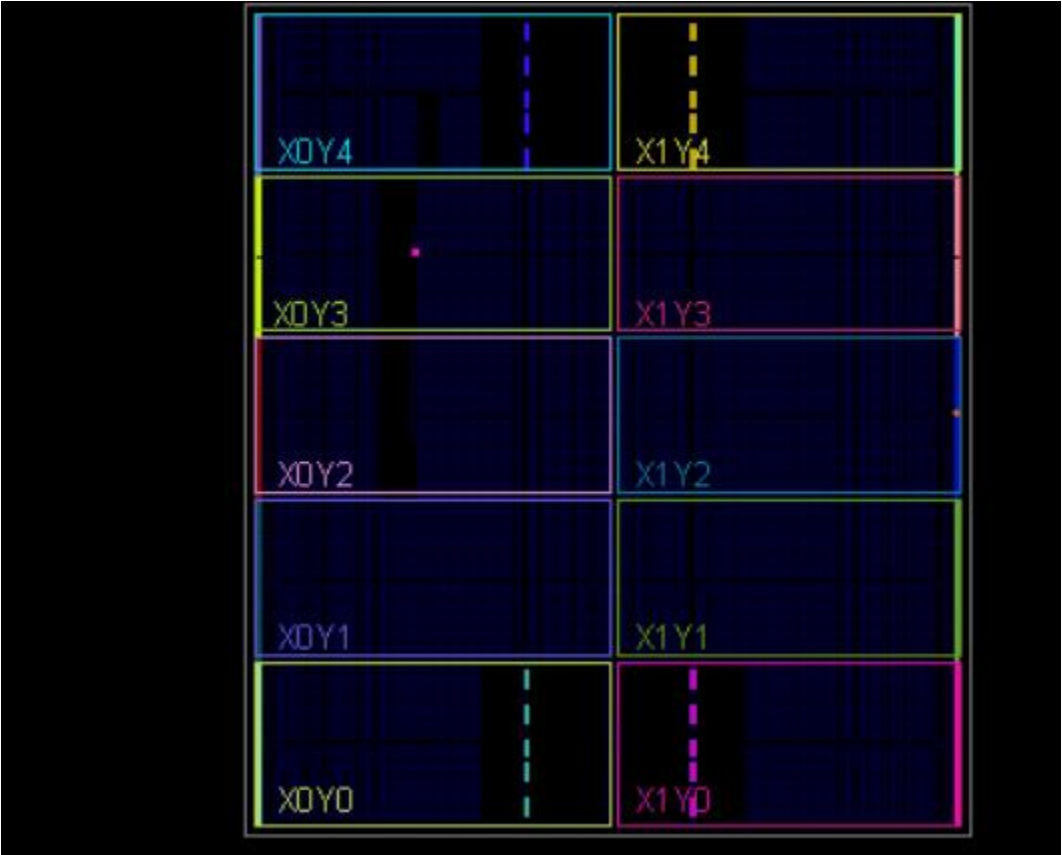

## 7.RTL design

### 1. Baud gen

```
BAUD.v  [icon] [X]
1  module baudrate_gen #(
2      parameter BAUDRATE = 9600,
3      parameter CLK_FREQ = 100_000_000
4  )(
5      input clk,
6      input reset,
7      output reg tick
8  );
9
10
11      localparam FINAL_TICK = (CLK_FREQ + (16*BAUDRATE - 1)) / (16*BAUDRATE);
12
13      reg [15:0] counter;
14
15      always @(posedge clk or posedge reset) begin
16          if (reset) begin
17              tick    <= 0;
18              counter <= 0;
19          end else if (counter == (FINAL_TICK - 1)) begin
20              counter <= 0;
21              tick    <= 1;
22          end else begin
23              counter <= counter + 1;
24              tick    <= 0;
25          end
26      end
27  endmodule
28
29
```

## 2. RX

```

1      module uart_rx #(
2          parameter DATAWIDTH = 8,
3          parameter SB_TICK    = 16
4      ) (
5          input  clk,
6          input  rx_rst,
7          input  rx_en,
8          input  rx,
9          input  s_tick,
10         output reg [DATAWIDTH-1:0] dout,
11         output reg rx_done,
12         output reg rx_busy,
13         output reg rx_error
14     );
15
16     localparam [1:0] IDLE = 2'b00,
17                    START = 2'b01,
18                    DATA = 2'b10,
19                    STOP  = 2'b11;
20
21     reg [1:0] state_reg, state_next;
22     reg [DATAWIDTH-1:0] data_reg, data_next;
23     reg [$clog2(DATAWIDTH)-1:0] n_reg, n_next;
24     reg [$clog2(SB_TICK)-1:0] s_reg, s_next;
25
26     always @(posedge clk or posedge rx_rst) begin
27         if (rx_rst) begin
28             state_reg <= IDLE;
29             data_reg  <= 0;
30             n_reg     <= 0;
31             s_reg     <= 0;
32             dout      <= 0;
33             rx_done   <= 0;
34             rx_busy   <= 0;
35             rx_error  <= 0;
36         end else begin
37             state_reg <= state_next;
38             data_reg  <= data_next;
39             n_reg     <= n_next;
40             s_reg     <= s_next;
41             dout      <= data_reg;
42         end
43     end
44
45     always @* begin
46         state_next = state_reg;
47         data_next  = data_reg;
48         n_next     = n_reg;
49         s_next     = s_reg;
50         rx_done    = 1'b0;
51         rx_busy    = (state_reg != IDLE);
52         rx_error   = 1'b0;
53
54         if (rx_en) begin
55             case (state_reg)
56                 IDLE: if (~rx) begin
57                     state_next = START;
58                     s_next     = 0;

```

RX.v

```
38         data_reg <= data_next;
39         n_reg    <= n_next;
40         s_reg    <= s_next;
41         dout     <= data_reg;
42     end
43 end
44
45 always @* begin
46     state_next = state_reg;
47     data_next  = data_reg;
48     n_next     = n_reg;
49     s_next     = s_reg;
50     rx_done    = 1'b0;
51     rx_busy    = (state_reg != IDLE);
52     rx_error   = 1'b0;
53
54     if (rx_en) begin
55         case (state_reg)
56             IDLE: if (~rx) begin
57                     state_next = START;
58                     s_next     = 0;
59                 end
60             START: if (s_tick) begin
61                     if (s_reg == 7) begin
62                         state_next = DATA;
63                         s_next     = 0;
64                         n_next     = 0;
65                     end else s_next = s_reg + 1;
66                 end
67             DATA: if (s_tick) begin
68                     if (s_reg == 15) begin
69                         data_next = {rx, data_reg[DATAWIDTH-1:1]};
70                         s_next     = 0;
71                         if (n_reg == (DATAWIDTH-1))
72                             state_next = STOP;
73                         else
74                             n_next = n_reg + 1;
75                     end else s_next = s_reg + 1;
76                 end
77             STOP: if (s_tick) begin
78                     if (s_reg == (SB_TICK-1)) begin
79                         if (~rx) rx_error = 1'b1;
80                         state_next = IDLE;
81                         rx_done    = 1'b1;
82                     end else s_next = s_reg + 1;
83                 end
84         endcase
85     end
86 end
87 endmodule
```



### 3. TX

```
TX.v  [icon] [X]
1  module uart_tx #(
2      parameter DATAWIDTH = 8,
3      parameter SB_TICK    = 16
4  )(
5      input  clk,
6      input  tx_rst,
7      input  tx_en,
8      input  tx_start,
9      input  [DATAWIDTH-1:0] din,
10     input  s_tick,
11     output reg tx,
12     output reg tx_done,
13     output reg tx_busy
14 );
15
16     localparam [1:0] IDLE = 2'b00,
17                     START = 2'b01,
18                     DATA = 2'b10,
19                     STOP  = 2'b11;
20
21     reg [1:0] state, state_n;
22     reg [$clog2(SB_TICK)-1:0] s_reg, s_n;
23     reg [$clog2(DATAWIDTH)-1:0] n_reg, n_n;
24     reg [DATAWIDTH-1:0] b_reg, b_n;
25     reg tx_n, tx_done_n;
26
27     always @(posedge clk or posedge tx_rst) begin
28         if (tx_rst) begin
29             state    <= IDLE;
30             s_reg    <= 0;
31             n_reg    <= 0;
32             b_reg    <= 0;
33             tx       <= 1'b1;
34             tx_done  <= 1'b0;
35             tx_busy  <= 1'b0;
36         end else begin
37             state    <= state_n;
38             s_reg    <= s_n;
39             n_reg    <= n_n;
40             b_reg    <= b_n;
41             tx       <= tx_n;
42             tx_done  <= tx_done_n;
43             tx_busy  <= (state_n != IDLE);
44         end
45     end
46
47     always @* begin
48         state_n    = state;
49         s_n        = s_reg;
50         n_n        = n_reg;
51         b_n        = b_reg;
52         tx_n       = tx;
53         tx_done_n  = 1'b0;
54
55         if (tx_en) begin
56             case (state)
57                 IDLE: begin
58                     tx_n = 1'b1;
```

TX.v

```
52     tx_n      = tx;
53     tx_done_n = 1'b0;
54
55     if (tx_en) begin
56         case (state)
57             IDLE: begin
58                 tx_n = 1'b1;
59                 if (tx_start) begin
60                     b_n = din;
61                     s_n = 0;
62                     state_n = START;
63                 end
64             end
65             START: begin
66                 tx_n = 1'b0;
67                 if (s_tick) begin
68                     if (s_reg == SB_TICK-1) begin
69                         s_n = 0;
70                         n_n = 0;
71                         state_n = DATA;
72                     end else s_n = s_reg + 1;
73                 end
74             end
75             DATA: begin
76                 tx_n = b_reg[n_reg];
77                 if (s_tick) begin
78                     if (s_reg == SB_TICK-1) begin
79                         s_n = 0;
80                         if (n_reg == DATAWIDTH-1)
81                             state_n = STOP;
82                     else
83                         n_n = n_reg + 1;
84                     end else s_n = s_reg + 1;
85                 end
86             end
87             STOP: begin
88                 tx_n = 1'b1;
89                 if (s_tick) begin
90                     if (s_reg == SB_TICK-1) begin
91                         state_n = IDLE;
92                         tx_done_n = 1'b1;
93                         s_n = 0;
94                     end else s_n = s_reg + 1;
95                 end
96             end
97         endcase
98     end
99 end
100 endmodule
```

#### 4. APBUART

```
apduart.v  + X
1  module apb_uart #(
2      parameter DATAWIDTH = 8,
3      parameter CLK_FREQ   = 100_000_000
4  )(
5      input  wire          PCLK,
6      input  wire          PRESETn,
7      input  wire [31:0] PADDR,
8      input  wire          PSEL,
9      input  wire          PENABLE,
10     input  wire          PWRITE,
11     input  wire [31:0] PWDATA,
12     output reg [31:0] PRDATA,
13     output reg          PREADY,
14     input  wire          rx,
15     output wire          tx
16 );
17
18     reg          tx_en, rx_en;
19     reg          tx_rst, rx_rst;
20     reg [DATAWIDTH-1:0] tx_data_reg;
21     wire [DATAWIDTH-1:0] rx_data_wire;
22     wire tx_done, tx_busy;
23     wire rx_done, rx_busy, rx_error;
24     reg [31:0] bauddiv_reg;
25     reg tx_start_pulse;
26
27     wire s_tick;
28     baudrate_gen #(
29         .BAUDRATE (9600),
30         .CLK_FREQ (CLK_FREQ)
31     ) baud_inst (
32         .clk      (PCLK),
33         .reset    (~PRESETn),
34         .tick     (s_tick)
35     );
36
37     uart_tx #(
38         .DATAWIDTH(DATAWIDTH)
39     ) tx_inst (
40         .clk      (PCLK),
41         .tx_rst   (tx_rst),
42         .tx_en    (tx_en),
43         .tx_start (tx_start_pulse),
44         .din      (tx_data_reg),
45         .s_tick   (s_tick),
46         .tx       (tx),
47         .tx_done  (tx_done),
48         .tx_busy  (tx_busy)
49     );
50
51     uart_rx #(
52         .DATAWIDTH(DATAWIDTH)
```

```

50
51     uart_rx #(
52         .DATAWIDTH(DATAWIDTH)
53     ) rx_inst (
54         .clk      (PCLK),
55         .rx_rst   (rx_rst),
56         .rx_en    (rx_en),
57         .rx       (rx),
58         .s_tick   (s_tick),
59         .dout     (rx_data_wire),
60         .rx_done  (rx_done),
61         .rx_busy  (rx_busy),
62         .rx_error (rx_error)
63     );
64
65     always @(posedge PCLK or negedge PRESETn) begin
66         if (!PRESETn) begin
67             {tx_en, rx_en, tx_rst, rx_rst} <= 4'b0;
68             tx_data_reg <= 0;
69             bauddiv_reg <= 0;
70             tx_start_pulse <= 0;
71             PREADY <= 0;
72             PRDATA <= 0;
73         end else begin
74             PREADY <= 0;
75             tx_start_pulse <= 0;
76             if (PSEL && PENABLE) begin
77                 PREADY <= 1'b1;
78                 if (PWRITE) begin
79                     case (PADDR[4:0])
80                         5'h00: {tx_en, rx_en, tx_rst, rx_rst} <= PWDATA[3:0];
81                         5'h02: begin
82                             tx_data_reg <= PWDATA[DATAWIDTH-1:0];
83                             tx_start_pulse <= 1'b1;
84                         end
85                         5'h04: bauddiv_reg <= PWDATA;
86                     endcase
87                 end else begin
88                     case (PADDR[4:0])
89                         5'h00: PRDATA <= {28'b0, tx_en, rx_en, tx_rst, rx_rst};
90                         5'h01: PRDATA <= {27'b0, rx_error, tx_done, rx_done, tx_busy, rx_busy};
91                         5'h02: PRDATA <= {24'b0, tx_data_reg};
92                         5'h03: PRDATA <= {24'b0, rx_data_wire};
93                         5'h04: PRDATA <= bauddiv_reg;
94                         default: PRDATA <= 32'b0;
95                     endcase
96                 end
97             end
98         end
99     end
100
101 endmodule

```

## 8. Test bench

### TX AND RX TESTBENCH

```
TB.v  + X
1  `timescale 1ns/1ps
2
3  module uart_tb;
4
5      localparam CLK_FREQ = 100_000_000;
6      localparam BAUDRATE = 9600;
7      localparam SB_TICK = 16;
8      localparam DATAWIDTH = 8;
9
10     reg clk;
11     reg reset;
12
13     wire s_tick;
14     wire tx;
15     reg tx_start;
16     reg tx_en, tx_rst;
17     wire tx_done;
18     wire tx_busy;
19     reg [DATAWIDTH-1:0] tx_data;
20
21     wire [DATAWIDTH-1:0] rx_data;
22     reg rx_en, rx_rst;
23     wire rx_done;
24     wire rx_busy;
25     wire rx_error;
26
27     initial clk = 0;
28     always #5 clk = ~clk;
29
30     baudrate_gen #(.BAUDRATE(BAUDRATE), .CLK_FREQ(CLK_FREQ))
31         baud (.clk(clk), .reset(reset), .tick(s_tick));
32
33     uart_tx #(.DATAWIDTH(DATAWIDTH), .SB_TICK(SB_TICK))
34         txu (
35             .clk(clk), .tx_rst(tx_rst), .tx_en(tx_en),
36             .tx_start(tx_start), .din(tx_data),
37             .s_tick(s_tick), .tx(tx),
38             .tx_done(tx_done), .tx_busy(tx_busy)
39         );
40
41     uart_rx #(.DATAWIDTH(DATAWIDTH), .SB_TICK(SB_TICK))
42         rxu (
43             .clk(clk), .rx_rst(rx_rst), .rx_en(rx_en),
44             .rx(tx), .s_tick(s_tick),
45             .dout(rx_data), .rx_done(rx_done),
46             .rx_busy(rx_busy), .rx_error(rx_error)
47         );
48
49     initial begin
50         reset = 1;
51         tx_rst = 1;
52         rx_rst = 1;
53         tx_en = 0;
54         rx_en = 0;
55         tx_data = 0;
56         tx_start = 0;
57         #50 reset = 0;
58         tx_rst = 0;
```

TB.v

```
35         .clk(clk), .tx_rst(tx_rst), .tx_en(tx_en),
36         .tx_start(tx_start), .din(tx_data),
37         .s_tick(s_tick), .tx(tx),
38         .tx_done(tx_done), .tx_busy(tx_busy)
39     );
40
41     uart_rx #(.DATAWIDTH(DATAWIDTH), .SB_TICK(SB_TICK))
42     rxu (
43         .clk(clk), .rx_rst(rx_rst), .rx_en(rx_en),
44         .rx(tx), .s_tick(s_tick),
45         .dout(rx_data), .rx_done(rx_done),
46         .rx_busy(rx_busy), .rx_error(rx_error)
47     );
48
49     initial begin
50         reset      = 1;
51         tx_rst     = 1;
52         rx_rst     = 1;
53         tx_en      = 0;
54         rx_en      = 0;
55         tx_data    = 0;
56         tx_start   = 0;
57         #50 reset = 0;
58         tx_rst     = 0;
59         rx_rst     = 0;
60         tx_en      = 1;
61         rx_en      = 1;
62         #1000;
63         tx_data = 8'hC1;
64         @(negedge clk) tx_start = 1;
65         @(negedge clk) tx_start = 0;
66         wait (rx_done);
67         $display("TX sent: %02h", tx_data);
68         $display("RX received: %02h | Error=%b", rx_data, rx_error);
69         if (rx_data == 8'hC1 && !rx_error)
70             $display("PASS: Successful Communication\n");
71         else
72             $display("FAIL: Expected Received Byte 0xC1\n");
73         #2000 $finish;
74     end
75 endmodule
76
```

## APBUART

```
apb_uart_tb.v
1 `timescale 1ns/1ps
2
3 module apb_uart_tb;
4
5     // Parameters
6     localparam DATAMWIDTH = 8;
7     localparam CLM_PERIOD = 10; // 100 MHz
8
9     // APB Signals
10    reg PCLK;
11    reg PRESETn;
12    reg PSEL;
13    reg PENABLE;
14    reg PWRITE;
15    reg [31:0] PADDR;
16    reg [31:0] PWDATA;
17    wire [31:0] PRDATA;
18    wire PREADY;
19
20    // UART Signals
21    reg rx;
22    wire tx;
23
24    // Test variables
25    reg [31:0] status;
26    reg [31:0] tx_data;
27    reg [31:0] rx_data;
28
29    // Instantiate the DUT
30    apb_uart #(
31        .DATAMWIDTH(DATAMWIDTH),
32        .CLM_FREQ(100_000_000)
33    ) dut (
34        .PCLK(PCLK),
35        .PRESETn(PRESETn),
36        .PADDR(PADDR),
37        .PSEL(PSEL),
38        .PENABLE(PENABLE),
39        .PWRITE(PWRITE),
40        .PWDATA(PWDATA),
41        .PRDATA(PRDATA),
42        .PREADY(PREADY),
43        .rx(rx),
44        .tx(tx)
45    );
46
47    // Clock generation
48    initial PCLK = 0;
49    always #((CLM_PERIOD/2) PCLK = ~PCLK;
50
51    // Reset generation
52    initial begin
53        PRESETn = 0;
54        #50;
55        PRESETn = 1;
56    end
57
58    // APB write task using negedge
59    task apb_write(input [4:0] addr, input [31:0] data);
60    begin
61        @(negedge PCLK); // Wait for falling edge (setup)
62        PSEL = 1;
63        PENABLE = 0;
64        PWRITE = 1;
65        PADDR = addr;
66        PWDATA = data;
67
68        @(negedge PCLK); // Access phase (sample will occur on DUT's rising edge)
69        PENABLE = 1;
70
71        @(negedge PCLK); // Transaction complete
72        PSEL = 0;
73        PENABLE = 0;
74    end
75    endtask
76
77    // APB read task using negedge
78    task apb_read(input [4:0] addr, output [31:0] data);
79    begin
80        @(negedge PCLK); // Setup phase
81        PSEL = 1;
82        PENABLE = 0;
83        PWRITE = 0;
84        PADDR = addr;
85
86        @(negedge PCLK); // Access phase
87        PENABLE = 1;
```

46 %



No issues found

## apb\_uart\_tb.v

```
51 // Reset generation
52 initial begin
53     PRESETn = 0;
54     $S0;
55     PRESETn = 1;
56 end
57
58 // APB write task using negedge
59 task apb_write(input [4:0] addr, input [31:0] data);
60 begin
61     @(negedge PCLK); // Wait for falling edge (setup)
62     PSEL = 1;
63     PENABLE = 0;
64     PWRITE = 1;
65     PADDR = addr;
66     PWDATA = data;
67
68     @(negedge PCLK); // Access phase (sample will occur on OUT's rising edge)
69     PENABLE = 1;
70
71     @(negedge PCLK); // Transaction complete
72     PSEL = 0;
73     PENABLE = 0;
74 end
75 endtask
76
77 // APB read task using negedge
78 task apb_read(input [4:0] addr, output [31:0] data);
79 begin
80     @(negedge PCLK); // Setup phase
81     PSEL = 1;
82     PENABLE = 0;
83     PWRITE = 0;
84     PADDR = addr;
85
86     @(negedge PCLK); // Access phase
87     PENABLE = 1;
88
89     @(negedge PCLK); // Sample data
90     data = PRDATA;
91
92     PSEL = 0;
93     PENABLE = 0;
94 end
95 endtask
96
97 // Test stimulus
98 initial begin
99     // Initialize signals
100     PSEL = 0;
101     PENABLE = 0;
102     PWRITE = 0;
103     PADDR = 0;
104     PWDATA = 0;
105     rx = 1'b1; // Idle state
106
107     @(negedge PRESETn); // Wait for reset release
108
109     // Enable UART TX/RX
110     apb_write(5'h00, 4'b1111); // tx_en, rx_en, tx_rst, rx_rst = 1
111
112     // Load TX data
113     apb_write(5'h02, 8'hA5); // transmit 8xA5
114
115     // Wait some time for transmission to finish
116     #5000;
117
118     // Read status register
119     apb_read(5'h01, status);
120     $display("Status Register: %h", status);
121
122     // Read TX data register
123     apb_read(5'h02, tx_data);
124     $display("TX Data Register: %h", tx_data);
125
126     // Read RX data register (assuming loopback for testing)
127     apb_read(5'h03, rx_data);
128     $display("RX Data Register: %h", rx_data);
129
130     $stop;
131 end
132
133 endmodule
```



## 9. Conclusion

The design and verification of the **APB UART wrapper** successfully demonstrated how a standard UART can be integrated into a system-on-chip environment through the AMBA APB interface. By separating the functionality into modular components — transmitter, receiver, baudrate generator, and APB interface — the design achieves both **clarity** and **scalability**.

The UART communication protocol was faithfully implemented using FSM-based Tx and Rx units, ensuring reliable transmission and reception of serial data with start, data, and stop bits. The inclusion of **oversampling in the receiver** improved robustness against timing mismatches, while the APB wrapper provided a straightforward register-mapped interface for software control.

Verification through a **loopback testbench** confirmed correct end-to-end operation, with data transmitted by the Tx accurately reconstructed by the Rx. The addition of status flags (`tx_busy`, `rx_busy`, `tx_done`, `rx_done`, `rx_error`) provided valuable system-level visibility and facilitated self-checking verification.

Overall, the project achieved its objectives by delivering a **functional, modular, and verifiable APB UART peripheral**. The design can be readily extended with advanced features such as FIFOs, parity checking, or interrupt support, making it suitable for integration into larger SoC designs.

This project successfully outlines the design and integration of a UART core with an AMBA APB interface. The modular design allows for flexible configuration, robust error detection, and clean SoC integration. The verification plan ensures correctness across all modules, and the design decisions balance complexity and functionality for practical use in embedded systems.

